

1. (a) For the circuit shown in Fig. P1, both junction diodes are identical, conducting $i_D = 10 \text{ mA}$ at $v_D = 0.7 \text{ V}$ and $i_D = 100 \text{ mA}$ at $v_D = 0.8 \text{ V}$. Find the value of R for which $V = 100 \text{ mV}$. (10%)
 (b) Illustrate the temperature dependence of the diode forward characteristic. (5%)

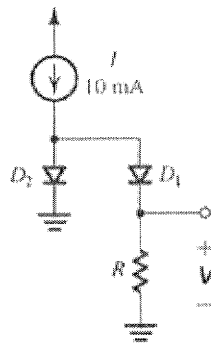


Fig. P1

2. The cascode amplifier shown in Fig. P2 is designed to provide an output swing of 1.9 V with a bias current of 0.5 mA . Assume $(W/L)_{1-4} = W/L$, and channel-length modulation and body effect are ignored.
 (a) What are the advantages and drawbacks of using a cascode current source? (2%)
 (b) Calculate V_{b1} , V_{b2} , and W/L . (9%)
 (c) What is the voltage gain if $L = 0.5 \mu\text{m}$? (6%)

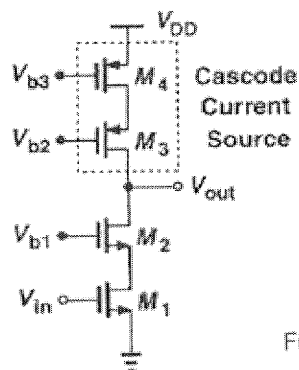


Fig. P2

3. Design a CMOS full-adder circuit with inputs A, B, and C, and two outputs S and C0 such that S is 1 if one or three inputs are 1, and C0 is 1 if two or more inputs are 1. Please sketch your circuit design with proper transistor sizing. Assume that for the basic inverter $n = 1.5$ and $p = 5$ and that the channel length is $0.25 \mu\text{m}$. (18%)

第 2 節

4. For the NMOS amplifier shown, assume the two capacitors are very large.

- (a) Draw the equivalent circuit with small signal model, (4%)
- (b) Specify the input resistance R_{in} , (3%)
- (c) Specify the output resistance R_{out} , (3%)
- (d) Derive the voltage gains v_o/v_{sig} , (4%)
- (e) Derive the 3-dB frequency f_{3dB} , (6%)

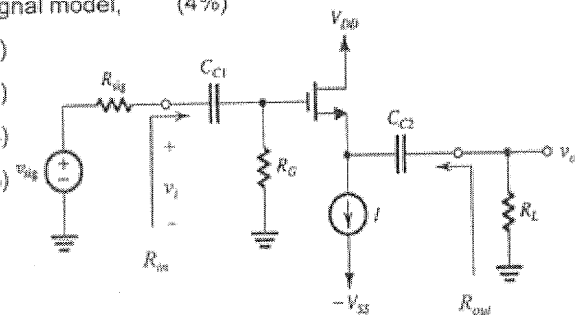


Fig. P4

5. A common-source amplifier with $g_m = 2 \text{ mA/V}$, $r_o = 50 \text{ k}\Omega$, $\chi = 0.2$, and $R_L = 50 \text{ k}\Omega$ has a $500\text{-}\Omega$ resistance R_S connected in the source lead.

- (a) Find R_{out} , (3%)
- (b) Determine the open-circuit voltage gain A_{v0} , (4%)
- (c) Determine the voltage gain A_v , (4%)
- (d) Determine the short-circuit trans-conductance G_m , (4%)

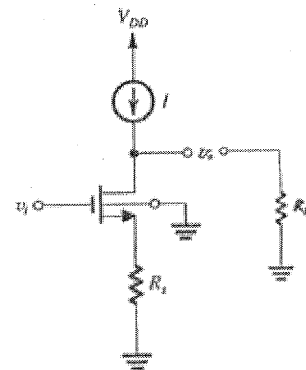


Fig. P5

6. For the following feedback circuit, the op amp has open-loop gain $\mu = 10^4 \text{ V/V}$, $R_{id} = 100 \text{ k}\Omega$, and $r_o = 1 \text{ k}\Omega$.

- (a) Specify the feedback type of the circuit, (3%)
- (b) Calculate the voltage gain v_o/v_s , (4%)
- (c) Calculate the input resistance R_{in} , (4%)
- (d) Calculate the output resistance R_{out} , (4%)

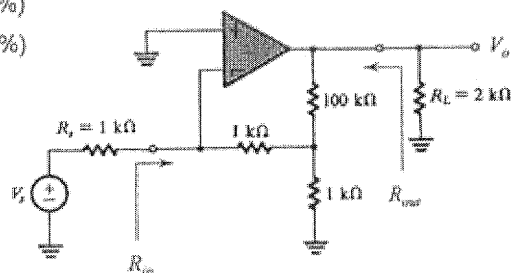


Fig. P6