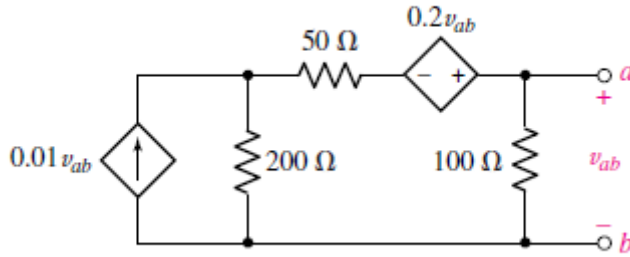


1.


49. Find the Thévenin equivalent of the two-terminal network shown in Fig. 5.91.



■ FIGURE 5.91

2.

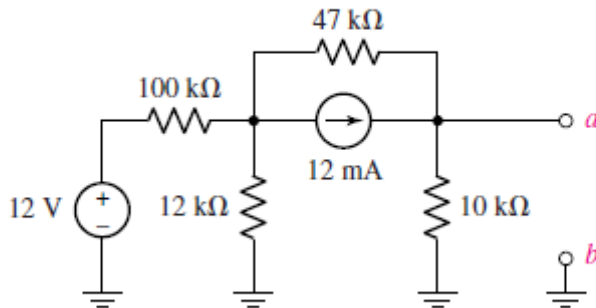
50. Find the Thévenin equivalent of the circuit in Fig. 5.92.



■ FIGURE 5.92

3.

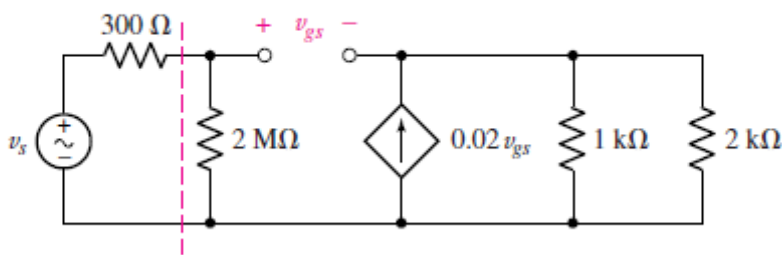
56. Find the Thévenin equivalent resistance seen by the 2 kΩ resistor in the circuit of Fig. 5.98. Ignore the dashed line in the figure.



■ FIGURE 5.98

4.

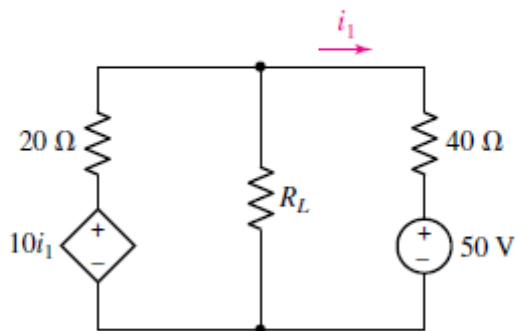
64. With reference to the circuit of Fig. 5.104: (a) determine that value of R_L to which a maximum power can be delivered, and (b) calculate the voltage across R_L then (+ reference at top).



■ FIGURE 5.104

5.

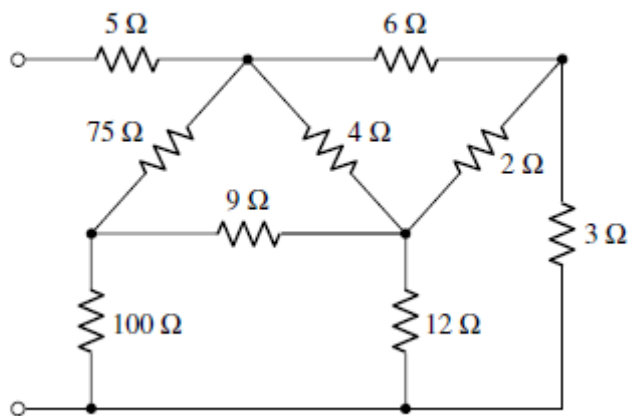
73. Use Y- Δ and Δ -Y transformations to find the input resistance of the network shown in Fig. 5.110.



■ FIGURE 5.110

6.

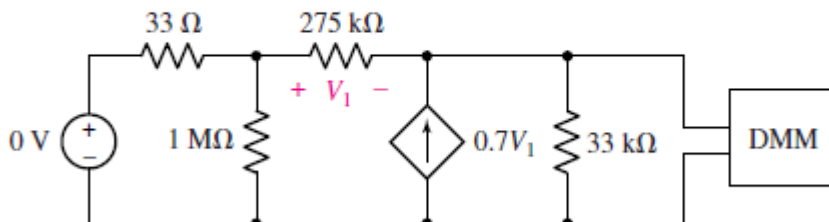
83. A DMM is connected to a resistor circuit as shown in Fig. 5.120. If the input resistance of the DMM is $1\text{ M}\Omega$, what value will be displayed if the DMM is measuring resistance?



■ FIGURE 5.120

7.

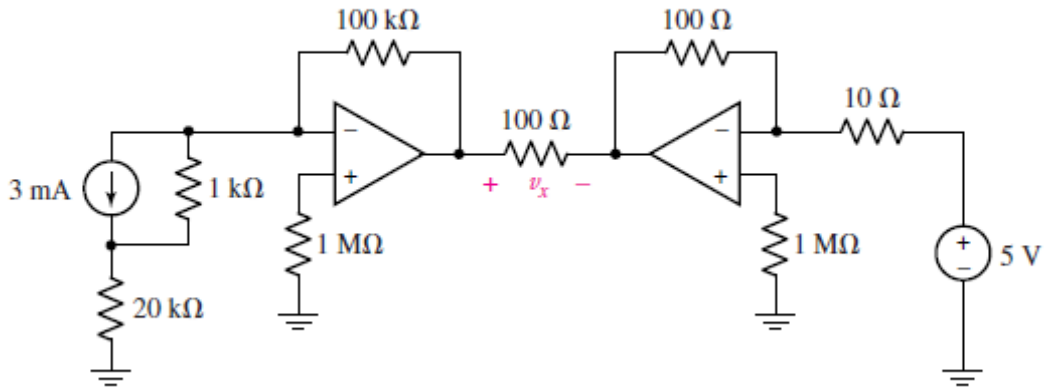
28. Compute v_x for the multiple op amp circuit of Fig. 6.59.



■ FIGURE 6.59

8.

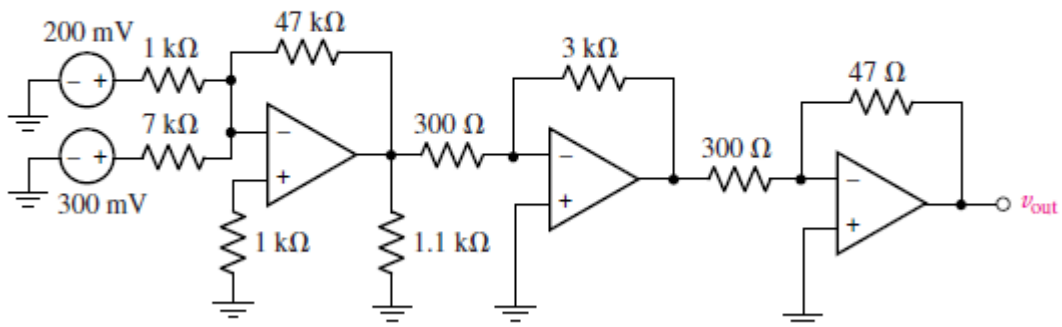
39. For the cascaded op amp circuit shown in Fig. 6.63, compute the output voltage of each stage.



■ FIGURE 6.63

9.

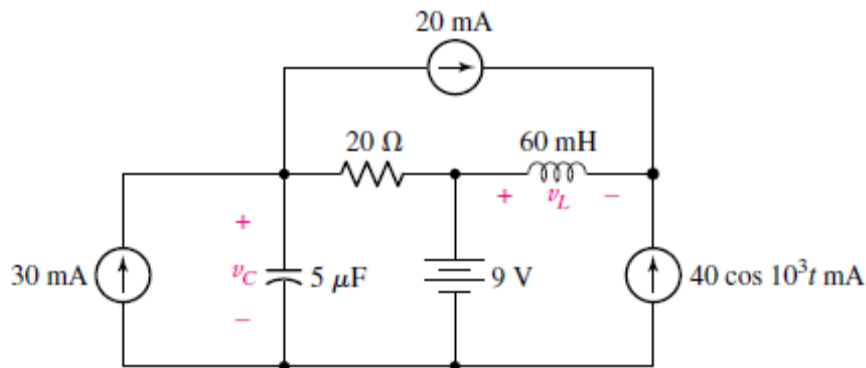
49. If it is assumed that all the sources in the circuit of Fig. 7.70 have been connected and operating for a very long time, use the superposition principle to find $v_C(t)$ and $v_L(t)$.



■ FIGURE 7.70

10.

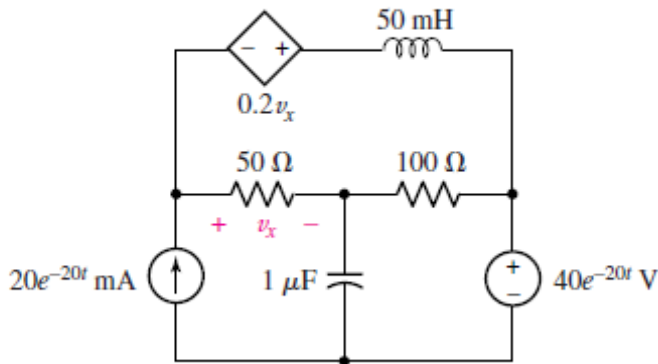
50. For the circuit of Fig. 7.71, assume no energy is stored at $t = 0$, and write a complete set of nodal equations.



■ FIGURE 7.71

11.

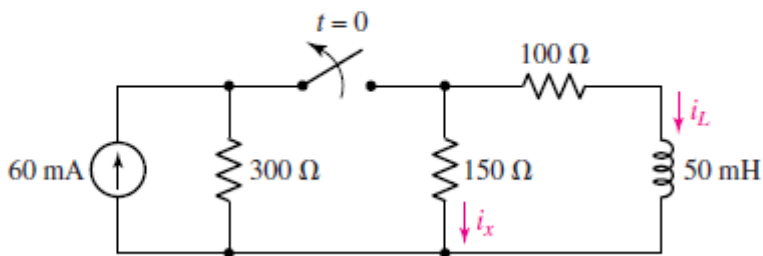
26. The switch in Fig. 8.66 opens at $t = 0$ after having been closed for an interminably long time. Find i_L and i_x at (a) $t = 0^-$; (b) $t = 0^+$; (c) $t = 300 \mu\text{s}$.



■ FIGURE 8.66

12.

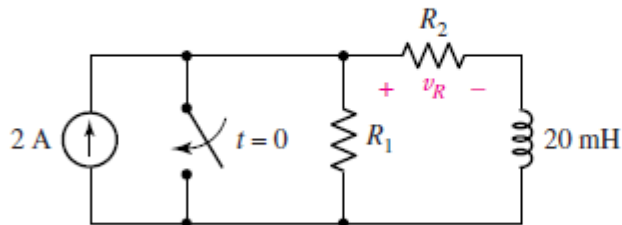
30. Select values for R_1 and R_2 in the circuit of Fig. 8.68 so that $v_R(0^+) = 10$ V and $v_R(1 \text{ ms}) = 5$ V.



■ FIGURE 8.68

13.

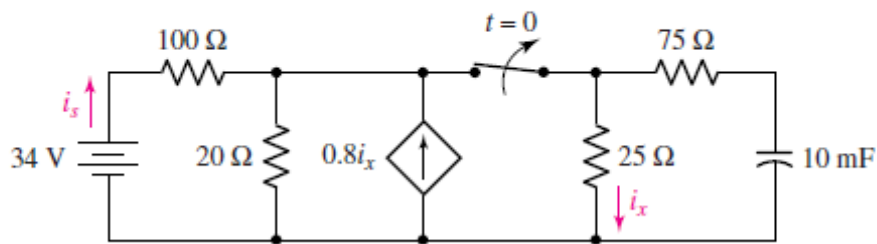
37. After being in the configuration shown for a long time, the switch in Fig. 8.74 is opened at $t = 0$. Determine values for (a) $i_s(0^-)$; (b) $i_x(0^-)$; (c) $i_x(0^+)$; (d) $i_s(0^+)$; (e) $i_x(0.4 \text{ s})$.



■ FIGURE 8.74

14.

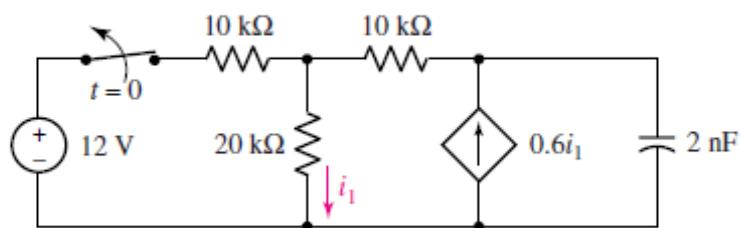
44. Find $i_1(t)$ for $t < 0$ and $t > 0$ in the circuit of Fig. 8.81.



■ FIGURE 8.81

15.

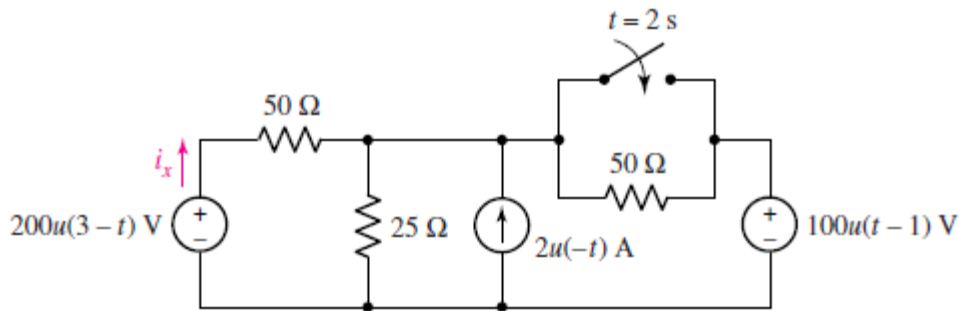
57. Find i_x in the circuit of Fig. 8.90 at 1 s intervals from $t = -0.5$ s to $t = 3.5$ s.



■ FIGURE 8.90

16.

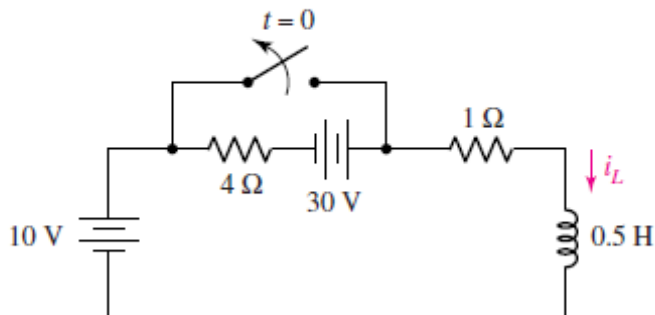
68. The switch shown in Fig. 8.100 has been closed for a long time. (a) Find i_L for $t < 0$. (b) Find $i_L(t)$ for all t after the switch opens at $t = 0$.



■ FIGURE 8.100

17.

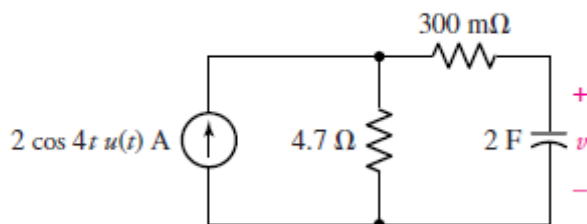
79. Find an expression for $v(t)$ in the circuit of Fig. 8.109 valid for all time.



■ FIGURE 8.109

18.

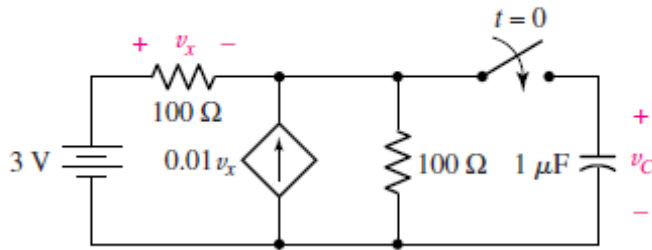
86. Find v_C for $t > 0$ in the circuit of Fig. 8.115.



■ FIGURE 8.115

19.

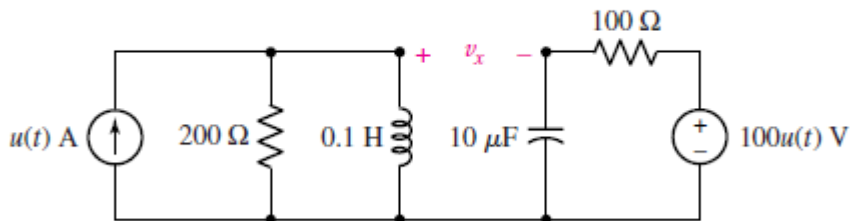
91. Find the first instant of time after $t = 0$ at which $v_x = 0$ in the circuit of Fig. 8.120.



■ FIGURE 8.120

20.

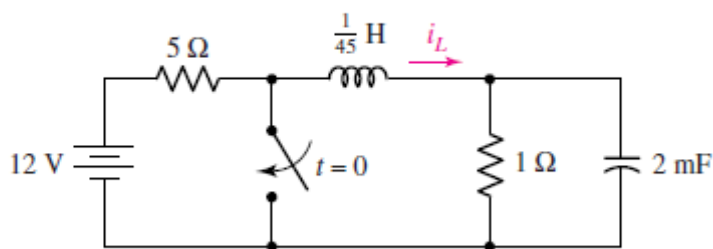
17. Find $i_L(t)$ for $t \geq 0$ in the circuit shown in Fig. 9.41.



■ FIGURE 9.41

21.

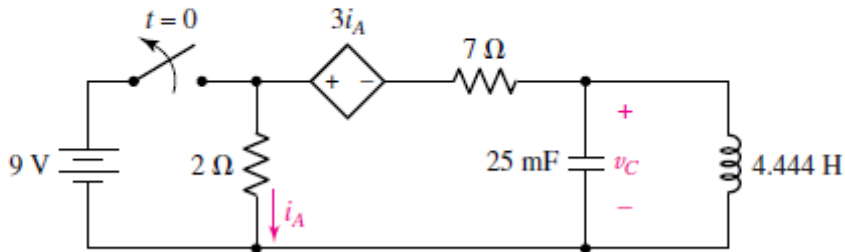
22. The switch in Fig. 9.45 was closed by the last crew aboard Mir before (at $t = 0$) it returned to earth. (a) Find $i_A(0^-)$. (b) Find $i_A(0^+)$. (c) Find $v_C(0^-)$. (d) Find the equivalent resistance in parallel with L and C for $t > 0$. (e) Find $i_A(t)$.



■ FIGURE 9.45

22.

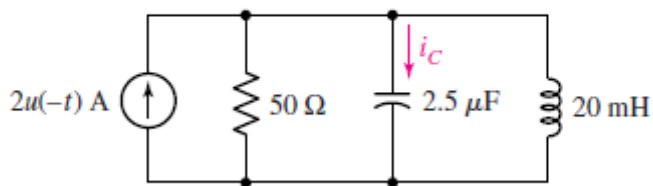
33. Find $i_C(t)$ for $t > 0$ in the circuit shown in Fig. 9.47.



■ FIGURE 9.47

23.

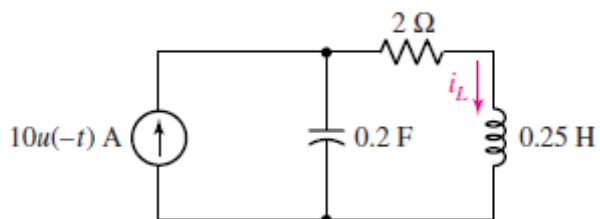
43. Find $i_L(t)$ for $t > 0$ in the circuit of Fig. 9.53.



■ FIGURE 9.53

24.

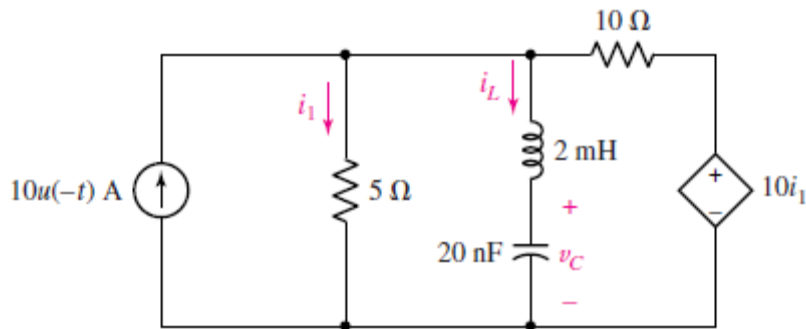
52. Find an expression for i_L as indicated in Fig. 9.58, valid for $t > 0$.



■ FIGURE 9.58

25.

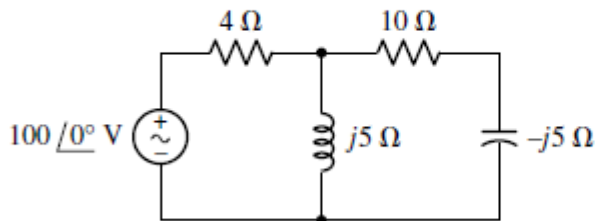
11. Find the average power being absorbed by each of the five circuit elements shown in Fig. 11.29.



■ FIGURE 11.29

26.

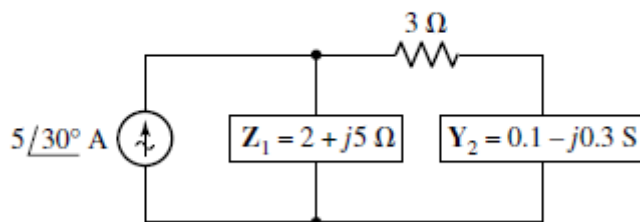
13. In the circuit shown in Fig. 11.31, find the average power being (a) dissipated in the 3Ω resistor; (b) generated by the source.



■ FIGURE 11.31

27.

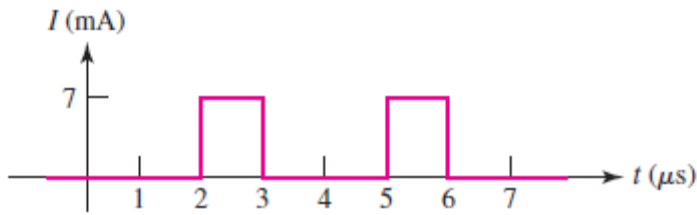
29. Determine the effective value of the waveform depicted in Fig. 11.42.



■ FIGURE 11.42

28.

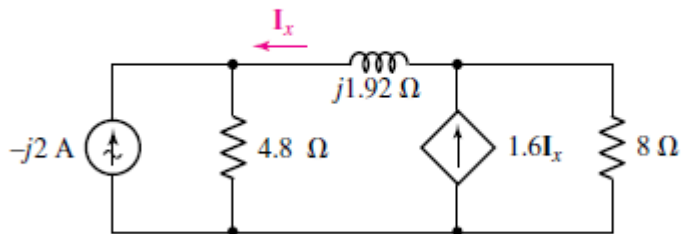
19. Find the average power supplied by the dependent source of Fig. 11.35.



■ FIGURE 11.35

29.

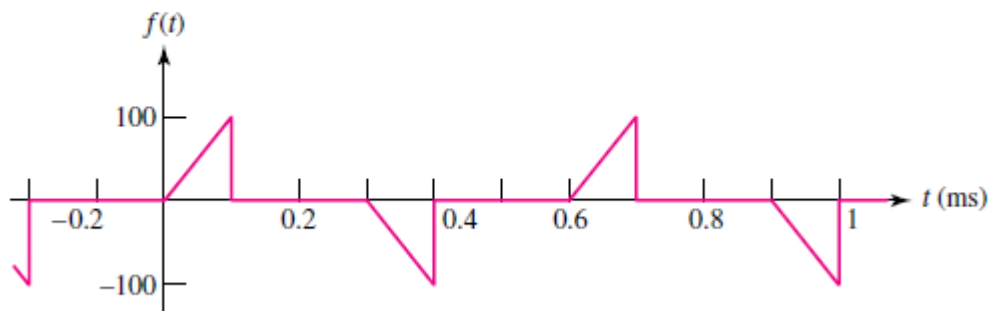
32. Find the effective value of (a) $g(t) = 2 + 3 \cos 100t + 4 \cos(100t - 120^\circ)$; (b) $h(t) = 2 + 3 \cos 100t + 4 \cos(101t - 120^\circ)$; (c) the waveform of Fig. 11.44.



■ FIGURE 11.44

30.

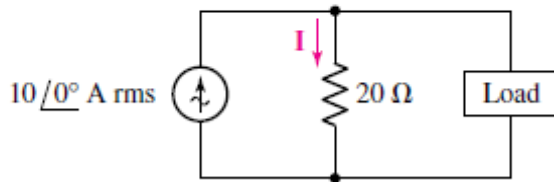
41. In Fig. 11.47, let $\mathbf{I} = 4/35^\circ$ A rms, and find the average power being supplied: (a) by the source; (b) to the $20\ \Omega$ resistor; (c) to the load. Find the apparent power being supplied: (d) by the source; (e) to the $20\ \Omega$ resistor; (f) to the load. (g) What is the load PF?



■ FIGURE 11.47

31.

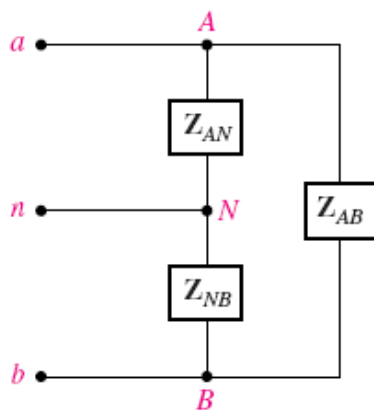
10. The 230/460 V rms 60 Hz three-wire system shown in Fig. 12.29 supplies power to three loads: load AN draws a complex power of $10/40^\circ$ kVA, load NB uses $8/10^\circ$ kVA, and load AB requires $4/-80^\circ$ kVA. Find the two line currents and the neutral current.



■ FIGURE 12.29

32.

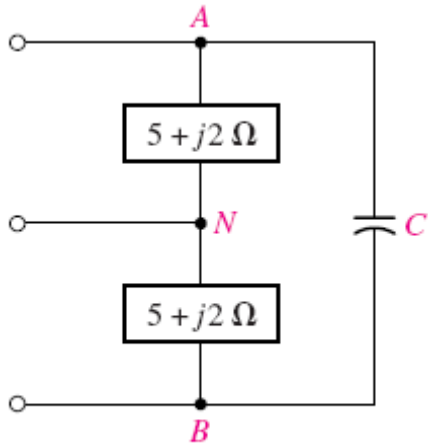
13. In the balanced three-wire single-phase system of Fig. 12.30, let $V_{AN} = 220$ V at 60 Hz. (a) What size should C be to provide a unity-power-factor load? (b) How many kVA does C handle?



■ FIGURE 12.30

33.

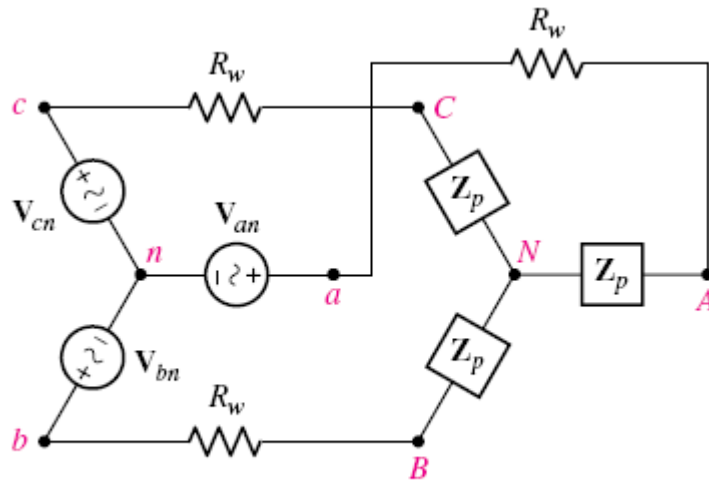
15. Figure 12.31 shows a balanced three-phase three-wire system with positive phase sequence. Let $V_{BC} = 120/60^\circ$ V and $R_w = 0.6 \Omega$. If the total load (including wire resistance) draws 5 kVA at PF = 0.8 lagging, find (a) the total power lost in the line resistance, and (b) V_{an} .



■ FIGURE 12.31

34.

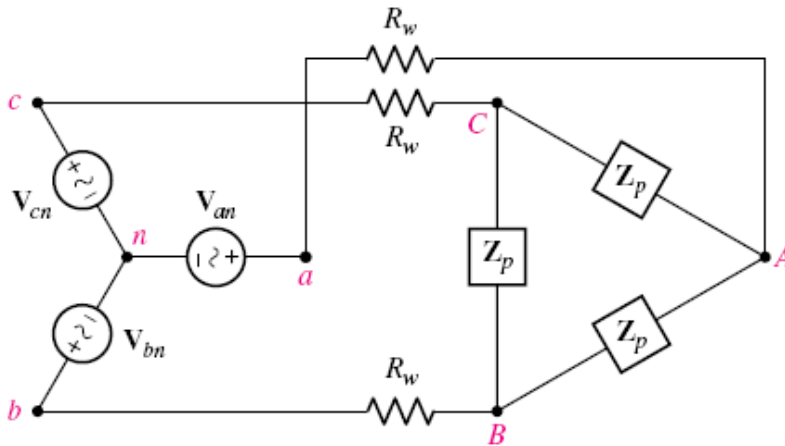
25. Figure 12.32 shows a balanced three-wire three-phase circuit. Let $R_w = 0$ and $V_{an} = 200\angle 60^\circ$ V. Each phase of the load absorbs a complex power, $S_p = 2 - j1$ kVA. If (+) phase sequence is assumed, find: (a) V_{bc} ; (b) Z_p ; (c) I_{aA} .



■ FIGURE 12.32

35.

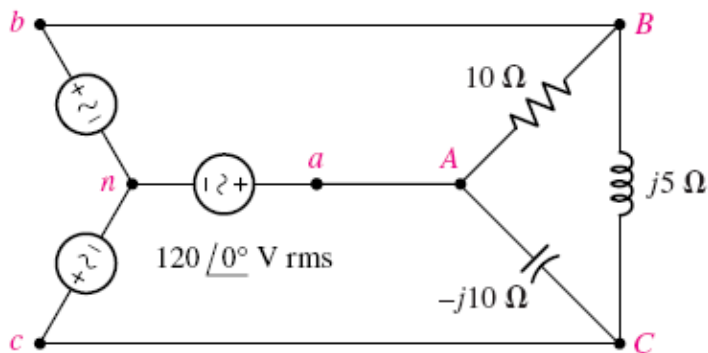29. The source in Fig. 12.33 is balanced and exhibits (+) phase sequence. Find (a) I_{aA} ; (b) I_{bB} ; (c) I_{cC} ; (d) the total complex power supplied by the source.



■ FIGURE 12.33